

## REPORT 3

### 7 SEGMENT DISPLAY

#### Function and Design :

There are 4 anodes present on the Basys-3 board. Each of which is connected to 7 cathodes. The combination of anode and cathodes makes 7 LEDs (A to G) present on a Basys-3 Board. 4 inputs b3 b2 b1 b0 are given to the decoder which represents the binary digits of the number which we have to display by using the 7 segment LED.

The decoder which is used is 4:16 decoder which returns 16 outputs representing 16 digits from 0 to 15. D0 represents 0, D1 represents 1 and so on.

The anode which we want to light up to give the single digit display is given a constant value 0 and rest all the anodes are given 1.

#### Conventions :

If the output at the cathode of any LED is 0, then it represents that the LED lights up and if the output is 1 then LED is off.

#### Example:

In representing 0 on display LED G didn't light up. Hence its value is 1 and rest all the values are 0.

| b3 b2 b1 b0 |     | A | B | C | D | E | F | G |
|-------------|-----|---|---|---|---|---|---|---|
| 0 0 0 0     | D0  | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 0 0 1     | D1  | 1 | 0 | 0 | 1 | 1 | 1 | 1 |
| 0 0 1 0     | D2  | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 0 1 1     | D3  | 0 | 0 | 0 | 0 | 1 | 1 | 0 |
| 0 1 0 0     | D4  | 1 | 0 | 0 | 1 | 1 | 0 | 0 |
| 0 1 0 1     | D5  | 0 | 1 | 0 | 0 | 1 | 0 | 0 |
| 0 1 1 0     | D6  | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 1 1 1     | D7  | 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 1 0 0 0     | D8  | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 0 0 1     | D9  | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1 0 1 0     | D10 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 0 1 1     | D11 | 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 1 0 0     | D12 | 0 | 1 | 1 | 0 | 0 | 0 | 1 |
| 1 1 0 1     | D13 | 1 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 1 1 0     | D14 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1 1 1 1     | D15 | 0 | 1 | 1 | 1 | 0 | 0 | 0 |

#### Test Cases:

Input:

b3 = 0

b2 = 0

b1 = 0

b0 = 1

Output

A = 1

B = 0

C = 0

D = 1

E = 1

F = 1

G = 1

**Test Case2:**

Input :

b3 = 0

b2 = 1

b1 = 0

b0 = 1

Output:

A = 0

B = 1

C = 0

D = 0

E = 1

F = 0

G = 0

Nikita Bhamu

Manoj Kumar