

# Lab Assignment 5

**Title:** Stopwatch

**Learning Objective:**

Learn (i) use of a pre-designed circuit (4 digit display, in this case) as a building block, (ii) creation of time reference.

**Specifications:**

Design a stopwatch and implement it on BASYS 3 board, using its 7-segment display and push buttons. Since the display has only 4 digits, assign these as follows - 1 digit for minutes, two digits for seconds and one digit for tenths of a second. Use three push buttons as follows.

- Start/Continue
- Pause
- Reset

**Details:**

The circuit will consist of a few counters, time reference and display (from assignment 4).

## ***A. Counters***

The design will be centered around an ensemble of four counters described below.

- A modulo 10 counter to count tenths of a second
- A modulo 10 counter to count unit digits of seconds
- A modulo 6 counter to count tens of seconds
- A modulo 10 counter to count minutes

The ensemble is driven by a 10 Hz timing reference. Provide for an enable input and a reset input. The enable input comes from a flip-flop/latch that is set to '1' when Start/Continue button is pressed and set to '0' when Pause button is pressed. Reset input comes from a push button.

The counters can be synchronous or asynchronous. In asynchronous counters, various bits may not change simultaneously, but the time delays will not be perceptible to the eye.

### ***B. Time reference***

100 MHz clock available on BASYS 3 board needs to be divided by  $10^7$  to get 10 Hz clock that updates tenths of a second. Note that a modulo N counter divides frequency by N. Recall that the display requires a clock in the range of 250 Hz to 4 KHz. Suppose you use 1 KHz clock for the display. Then you can first divide 100 MHz frequency by  $10^5$  to get 1 KHz and then divide it by 100 to get 10 Hz.